



The CD4017 decade counter advances its outputs (Q0 to Q6) with each clock pulse, driving LEDs for day indication through BC549 transistors. Pin 16 is connected to +5V, pin 8 to ground, and pin 13 also to ground. Pin 15 (reset) is connected to Q7 (pin 6) to ensure a weekly cycle. The emitters of all BC549 transistors are grounded, and their bases are driven by IC 555B through a 470 Ω resistor. Please refer to Tables 2 and 3 before assembly.

The circuit can be assembled on a general-purpose PCB or breadboard as shown in Fig. 3, starting with the power supply rails. Mount the two NE555 timers and the CD4017 IC with correct orientation.

WWW.EFYMAG.COM