

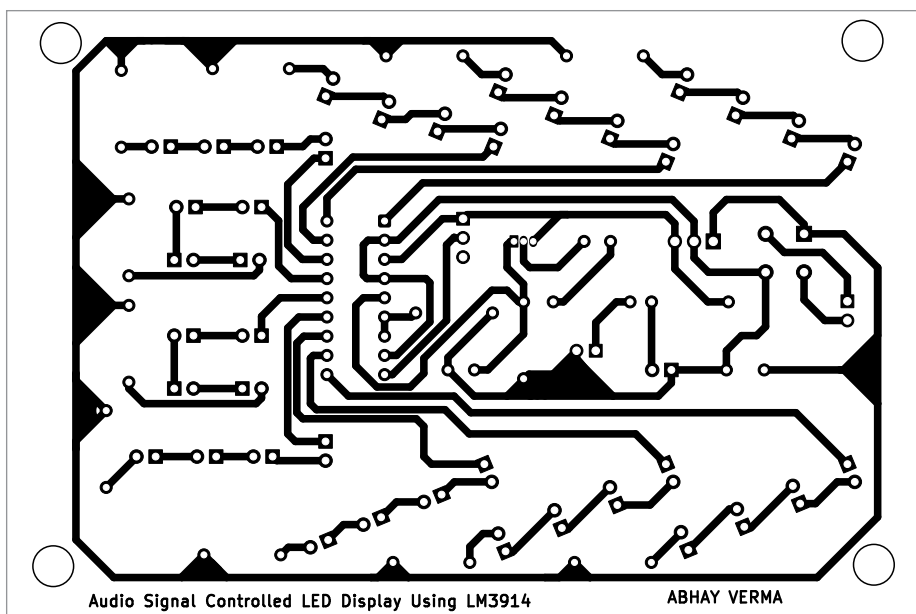


Fig. 3: Actual-size PCB pattern

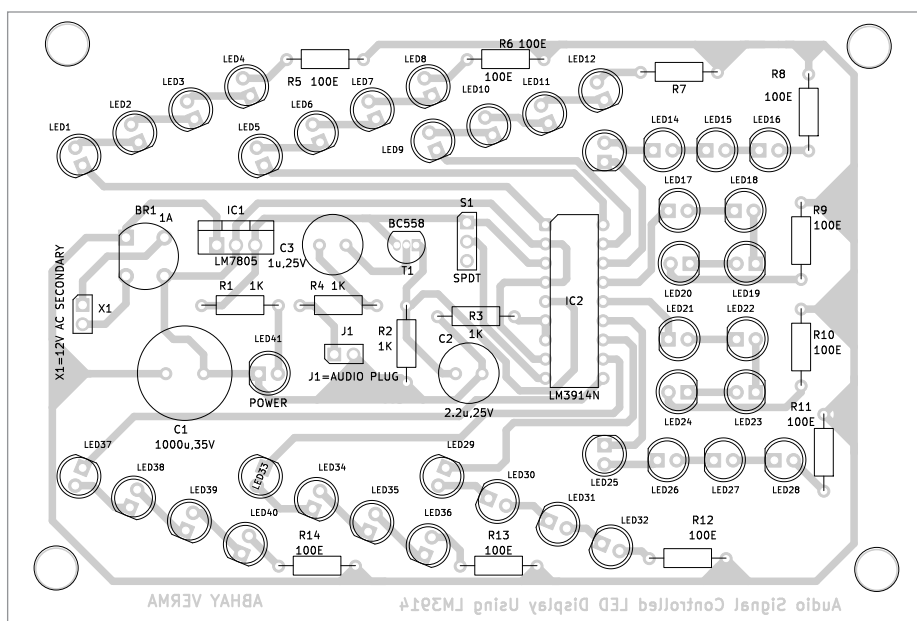


Fig. 4: Components layout

inside a suitable enclosure.

The footprints for connector CON1 and the transformer are not included on the PCB. These components should therefore be wired externally and secured inside the cabinet. Mount switch S1 and the power indicator LED41 on the front panel as per the circuit diagram. LEDs (LED1 through LED40) may be arranged in any desired pattern when the custom PCB is not used.

Use a short, shielded cable for the audio input to minimise hum and noise pickup. For continuous operation, fit the LM7805 voltage regulator with a small heat sink.

After assembly, power on the system and verify the regulated 5V DC output at the regulator. If LED41 glows, the power supply is functioning correctly. For testing, connect an audio source to the input jack and gradually increase the volume. The LEDs should illuminate in proportion to the audio signal level. **EFY**

Bonus. You can watch the video of the tutorial of this DIY project at: <https://www.electronicsforu.com/videos/slideshows/diy-audio-signal-controlled-led-display-using-lm3914>

S.C. Dwivedi is an electronics enthusiast and circuit designer at EFY

THE COMPLETE MAGAZINE ON OPEN SOURCE

OpenSource
ForYou

The latest from the Open Source world is here.

OpenSourceForU.com

Join the community at facebook.com/opensourceforu

Follow us on Twitter @OpenSourceForU